

BASIC ELECTRONICS – FINAL EXAM

Name. _____

Date. _____

Instructions. This is a timed test that must be completed in 15 minutes or less. It is not necessary to answer the bonus question. For all questions the following values apply:

$V_{in} = 12 \text{ VDC}$

All capacitors = $2 \mu\text{f}$

All coils = 2H

All resistors = $10\text{K } \Omega$

Resistance value of wire of any length = 15.001Ω

All mutual inductance will be 2H aiding

Questions.

1. (95 points) Calculate the total impedance for the circuit shown below: $Z =$ _____

2. (Bonus, 10 points) Calculate the resonant frequency of the circuit shown below. $f =$ _____

